

Chapter 4

Electrical Principles


Radio Mathematics

Volts, Amps, Resistance / Impedance

- Can't see
- Use equations to describe
- Graphs are pictures of equations
- Two types of graphs that show the same data in two different ways


Rectangular Coordinates

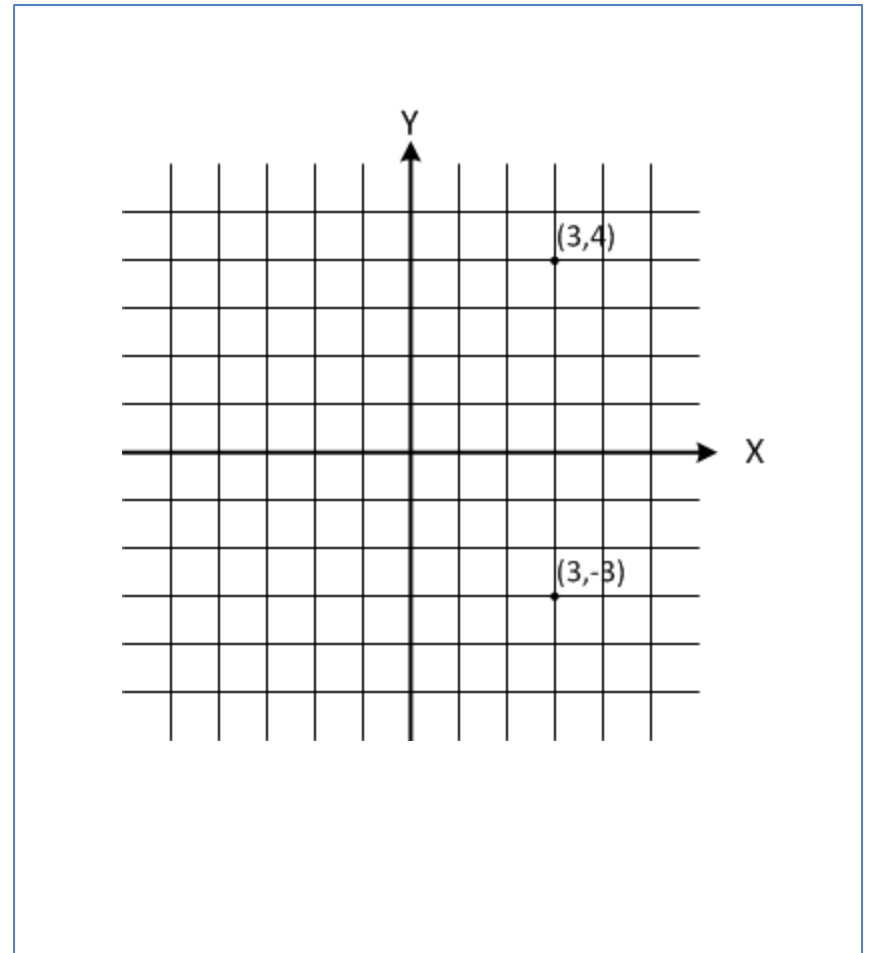- Graph is composed of two axis, horizontal (x) and vertical (y)
- The point (0,0) is called the origin
- Data point is identified as a (x,y) data pair




Polar Coordinates

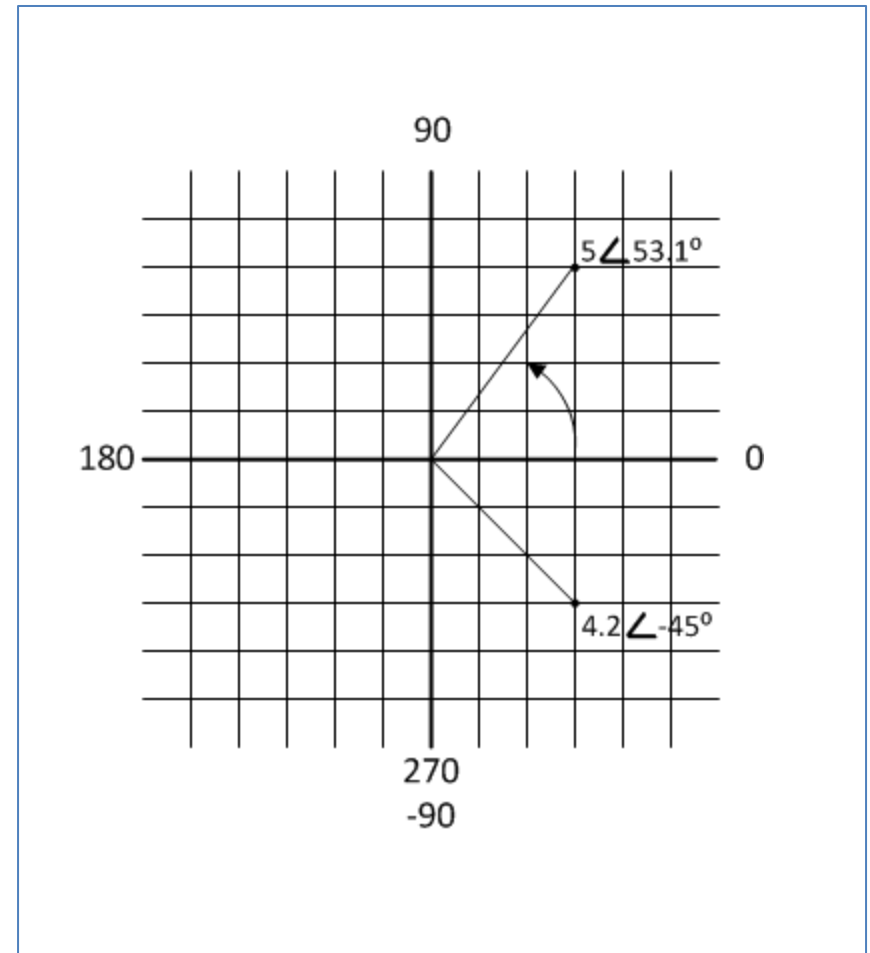- Graph is composed of a fixed point called a pole (analogous to origin)
- Data point (called a ray) is identified by a distance from the pole and an angle from the horizontal axis (counter clock wise is positive)
- Angles are measured in degrees and radians
 - One cycle / circle = 360 degrees = 2π radians (1 radian $\approx 57.3^\circ$)




Convert from Rectangular to Polar

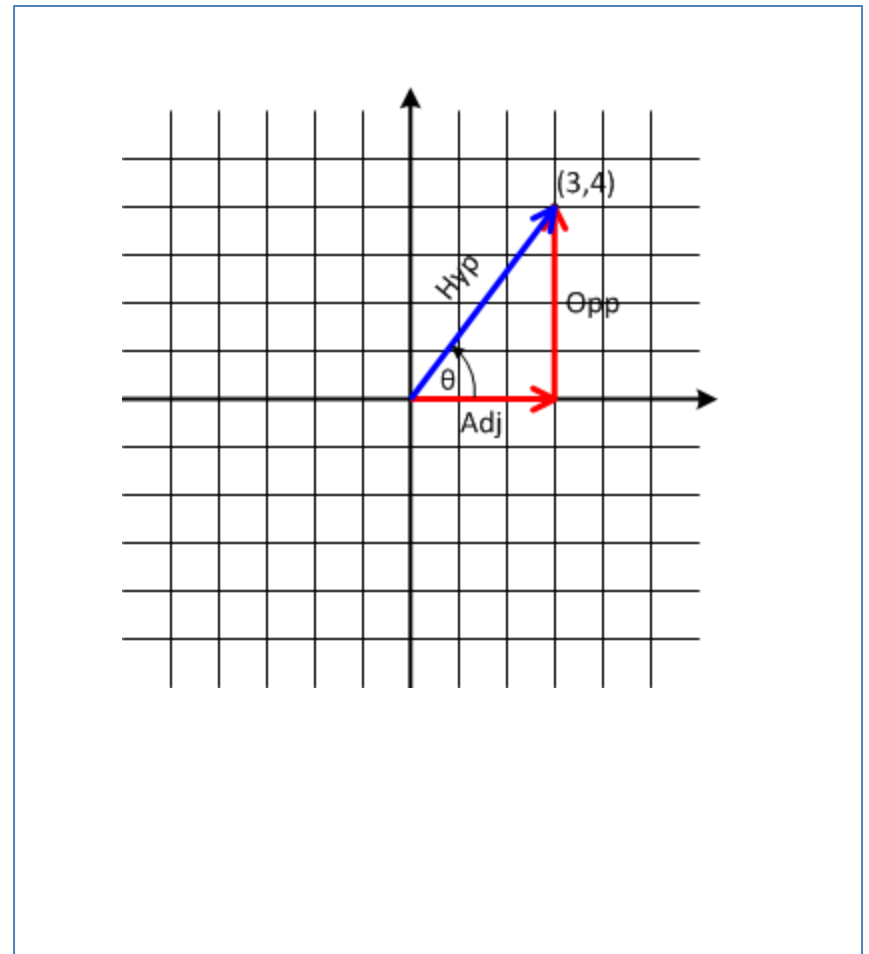- $Hyp = \sqrt{(Adj)^2 + (Opp)^2}$
- $\theta = \tan^{-1} (Opp / Adj)$



Convert from Polar to Rectangular

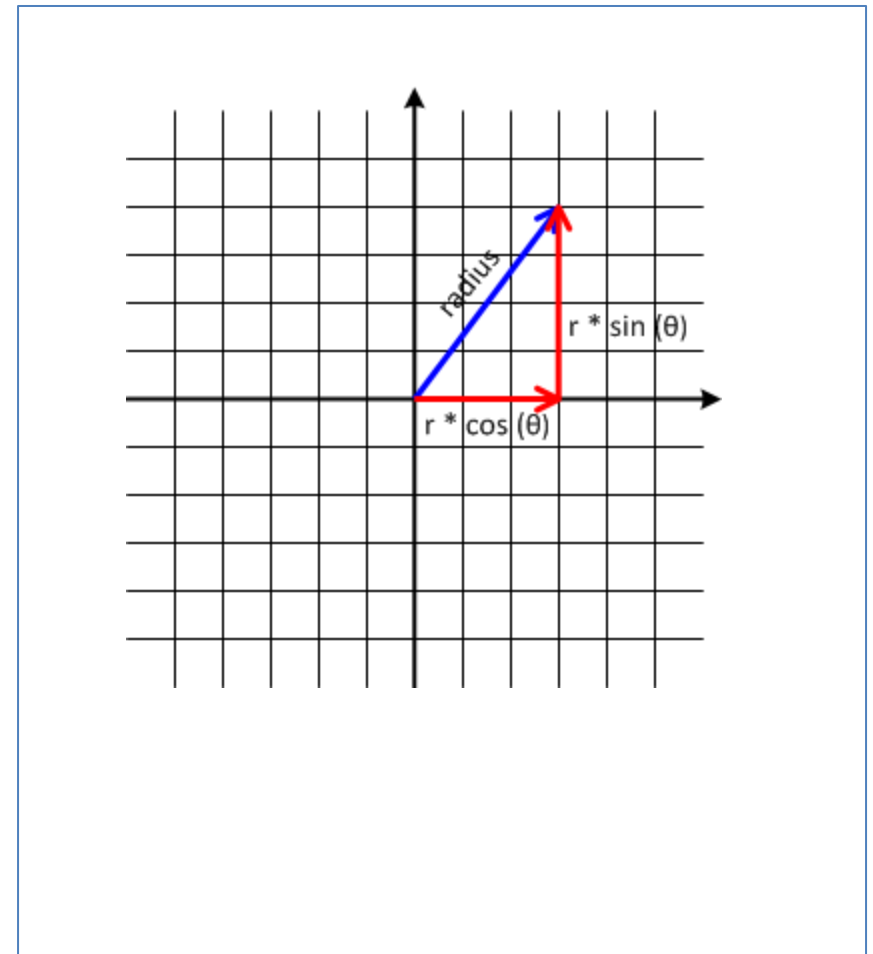- Radius (r) = Hyp
- Adj = $r * \cos \theta$
- Opp = $r * \sin \theta$



Complex numbers / coordinates

Imaginary numbers

➤ $\sqrt{36} = ?$

$$\sqrt{36} = 6$$


$$\sqrt{(4 * 9)} = \sqrt{4} * \sqrt{9} = 2 * 3 = 6$$

➤ $\sqrt{-25} = ?$

$$\sqrt{(25 * -1)} = \sqrt{25} * \sqrt{-1} = 5 * \sqrt{-1}$$

- $\sqrt{-1}$ is defined as “imaginary number”
- Mathematicians use i , Electrical Engineers use j because “ i ” is used to indicate instantaneous current

Complex Coordinates

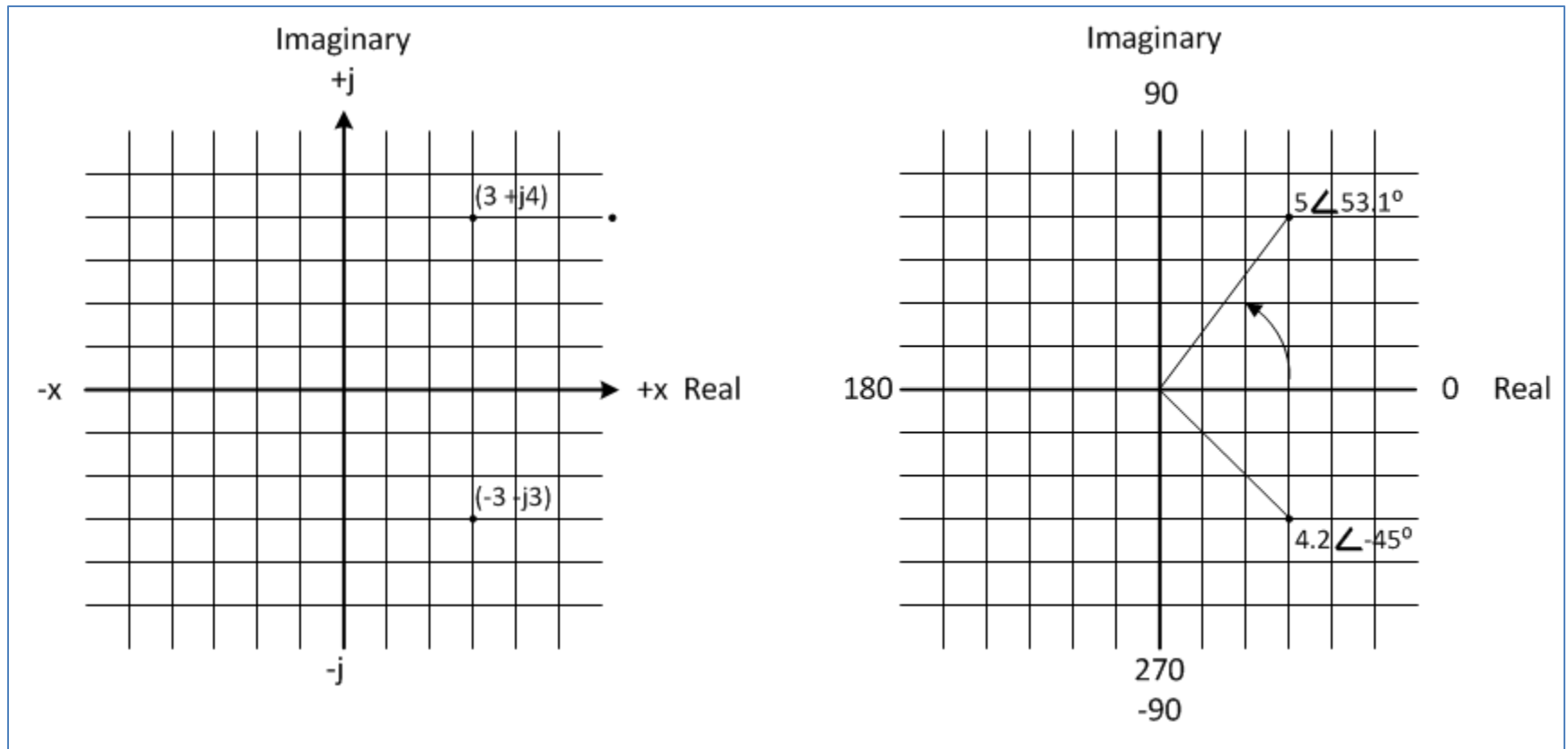

- Combine real & imaginary numbers
(real + j imaginary)


Convert Rectangular <> Polar

Rectangular to Polar

- $\text{Hyp} = \sqrt{(\text{Adj})^2 + (\text{Opp})^2}$
- $5 = \sqrt{(3)^2 + (4)^2}$
- $\theta = \tan^{-1} (\text{Opp} / \text{Adj})$
- $53.1^\circ = \tan^{-1} (4 / 3)$

Polar to Rectangular

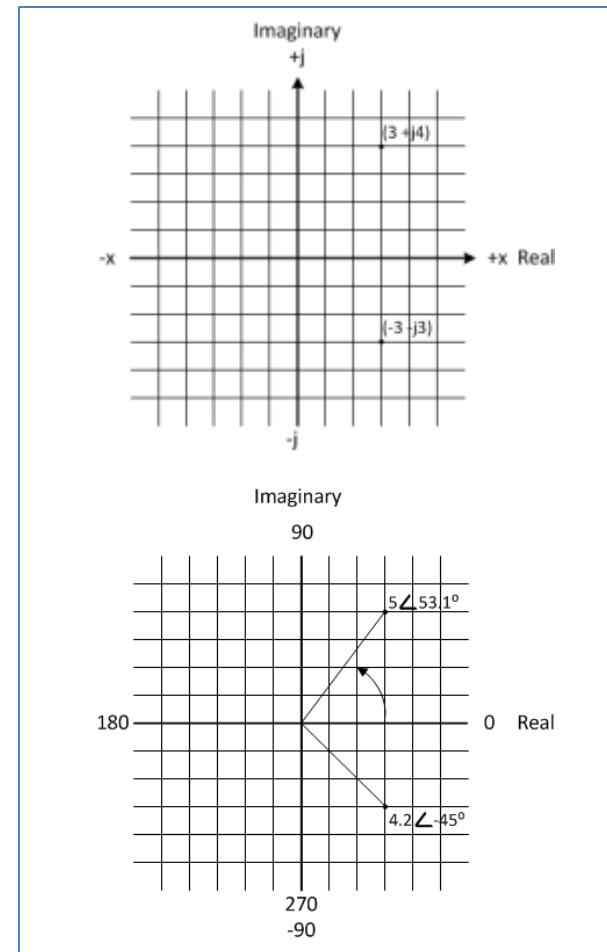- $\text{Adj} = r * \cos \theta$
- $3 = 4.2 * \cos(-45^\circ)$
- $\text{Opp} = r * \sin \theta$
- $-3 = 4.2 * \sin (-45^\circ)$



Complex numbers Math

Add/Subtract - Use Rectangular form

- $(a + j b) + (c + j d) = (a + c) + j (b + d)$
- $(2 + j3) + (4 + j1) = (6 + j4)$


Multiply/Divide - Use Polar form

- $a \angle \theta_1 * b \angle \theta_2 = (a * b) \angle (\theta_1 + \theta_2)$
- $a \angle \theta_1 / b \angle \theta_2 = (a / b) \angle (\theta_1 - \theta_2)$
- $6 \angle 45^\circ / 2 \angle 30^\circ = (6 / 2) \angle (45 - 30) = 3 \angle 15^\circ$

Electrical Principals

Electric and Magnetic fields

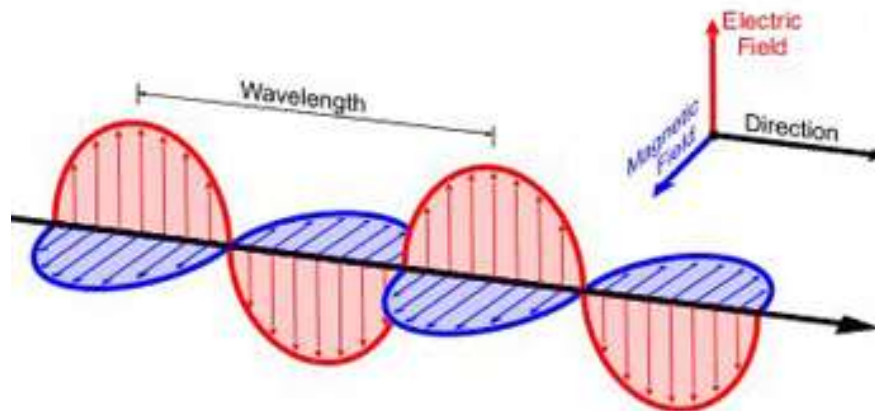- Introduced to E & M fields associated with antennas




RC and RL Time Constants

- Electrical energy
 - Can be detected as voltage differences between two points
 - Capacitors store and release electrical energy
 - Capacitors will resist a change in voltage
- Magnetic energy
 - Is detected by moving electrical charges (current)
 - Inductors store and release magnetic energy
 - Inductors will resist a change in current movement

Current / Magnetic field direction

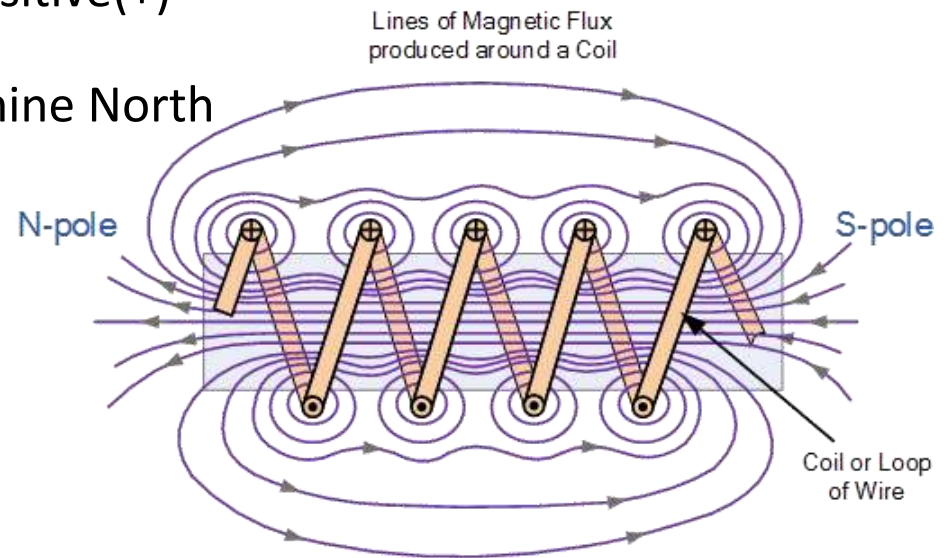- Electronics (Elect Engr) use “whole” or “conventional” current
 - Current flows positive (+) \rightarrow negative (-)
 - Use “Right Hand rule” to determine North
- Physics use “electron” current
 - Current flows negative (-) \rightarrow positive(+)
 - Use “Left Hand rule” to determine North






Time Constant

- RC circuit - The time it takes to charge (or discharge) a capacitor (V_C) depends on the size of the resistor
- RL circuit - The time it takes for current to increase (or decrease) through an inductor (i_L) also depends on the size of the resistor.


RC Circuit

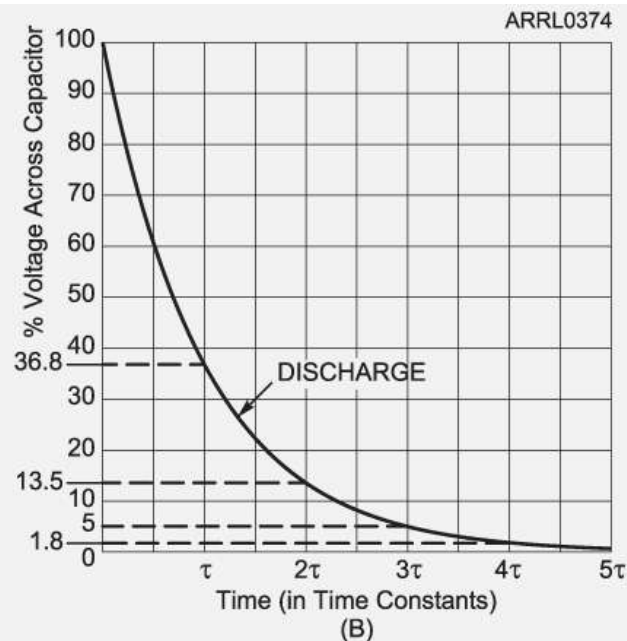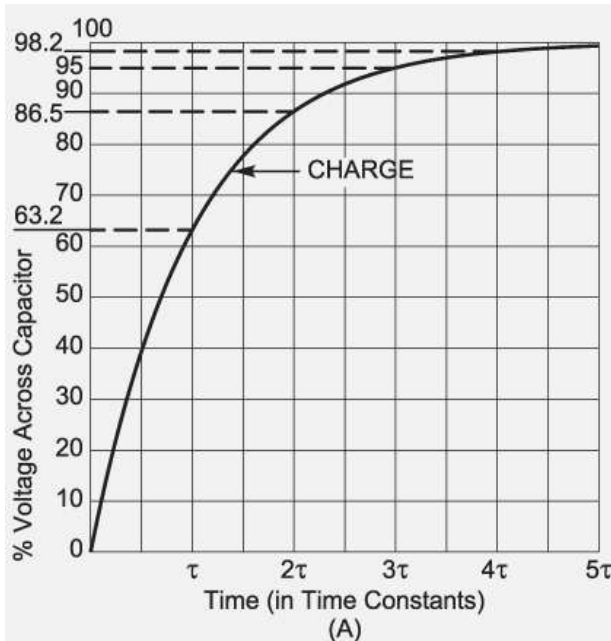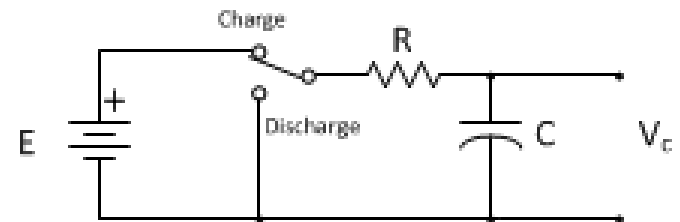- When charging a capacitor, $V_C(t) = E(1 - e^{-\frac{t}{\tau}})$ where $\tau = RC$
- When discharging a capacitor, $V_C(t) = E(e^{-\frac{t}{\tau}})$
- $e = 2.71828$ (base for natural logarithms)
- It takes approximately 5 time constants to charge to 99.3% (or discharge to 0.7%)




RL Circuit

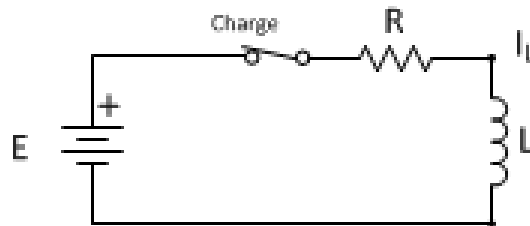- Building current through an inductor, $I_L(t) = \frac{E}{R} * (1 - e^{-\frac{t}{\tau}})$
where $\tau = L/R$
- When disrupting current through an inductor, $I_L(t) = \frac{E}{R} * (e^{-\frac{t}{\tau}})$
- It takes approximately 5 time constants to charge to 99.3% (or discharge to 0.7%)



Phase Angle

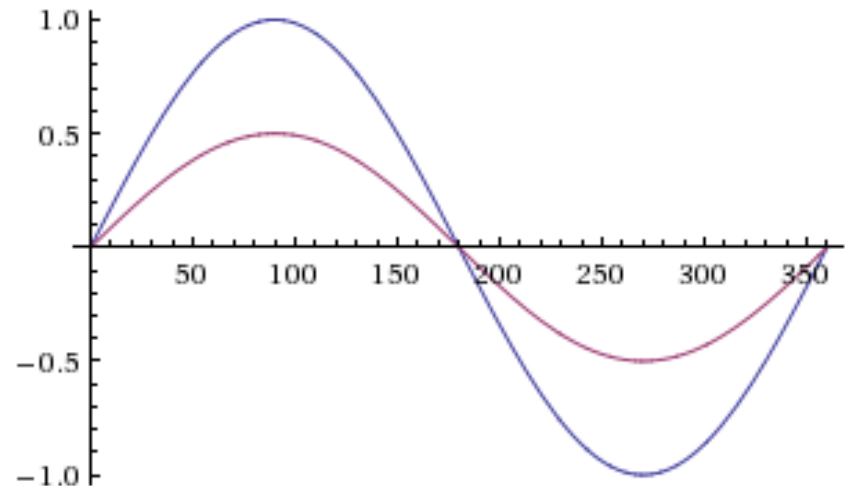- Phase Angle refers to time
 - 1 cycle of frequency $x = 1/x$ seconds
 - 1 cycle = 360°
 - Phase angle is measured between similar points on each waveform
- Resistors dissipate energy
 - voltage & current are “in phase”




Phase Angle

- Capacitors and Inductors store / release energy
 - Unlike in Resistors, voltage & current waveforms do NOT rise and fall together
- ELI the ICE man
 - Inductors – voltage (E) leads current (I)
 - Capacitors – current (I) leads voltage (E)

Voltage/Current Relationship in Capacitors


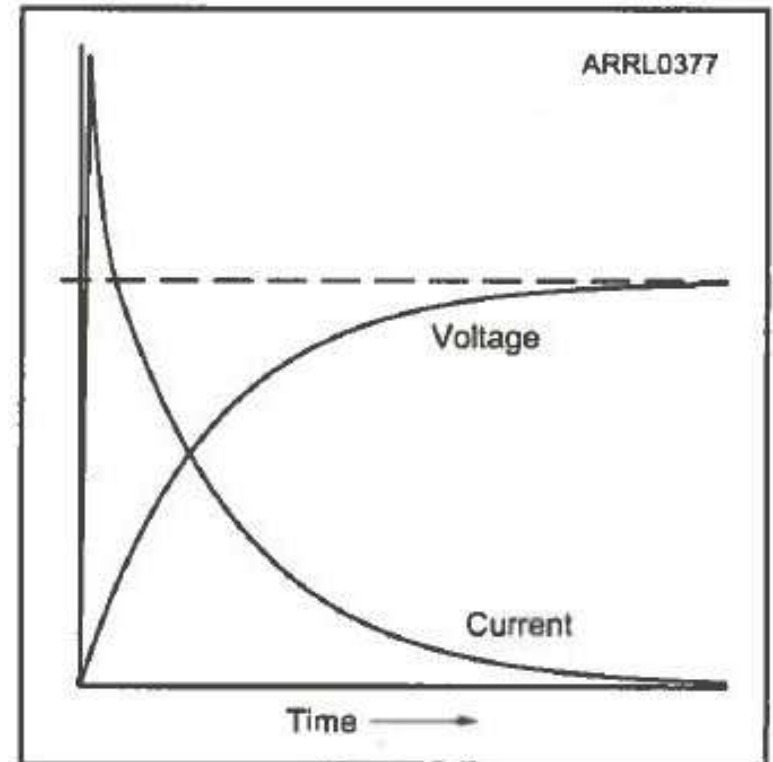
- Capacitors **resist** changes in voltage
- DC voltage / current
 - Physical example, filling a tank with air



AC Voltage/Current phase relationship in Capacitors



ICE - current LEADS voltage (V_C)

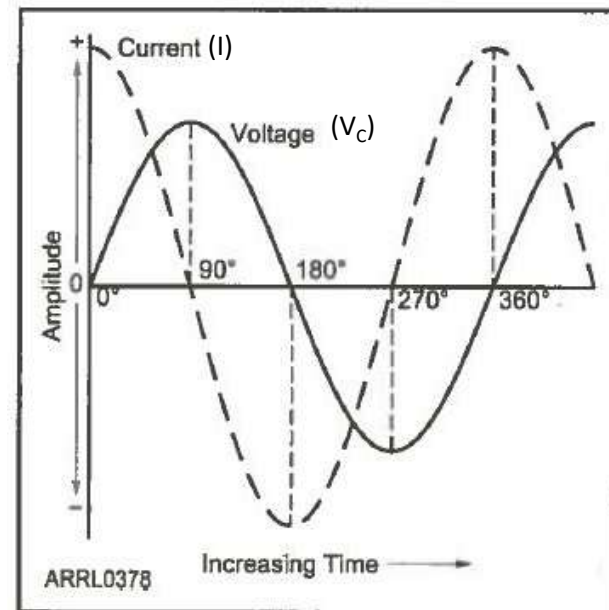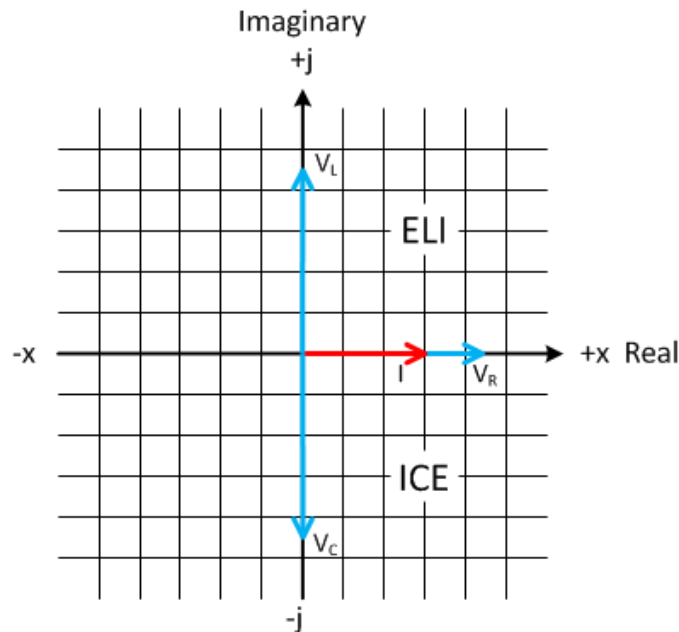- voltage (V_C) **LAGS** current
- (current is reference) phase angle is -90°




Electric (field strength) energy is stored and released twice each cycle

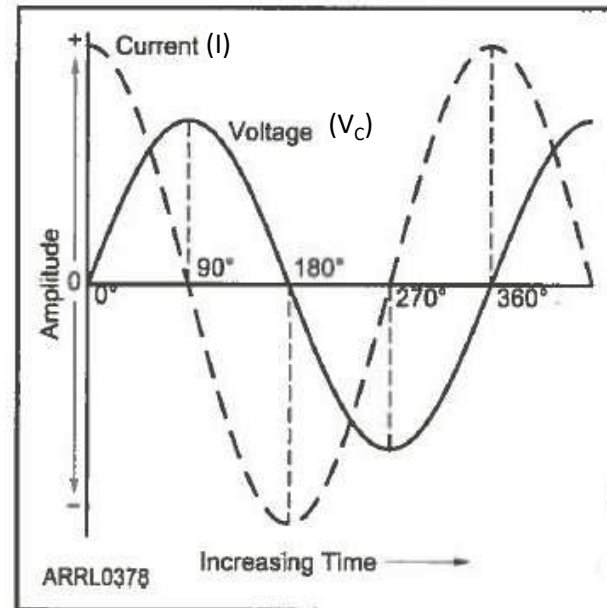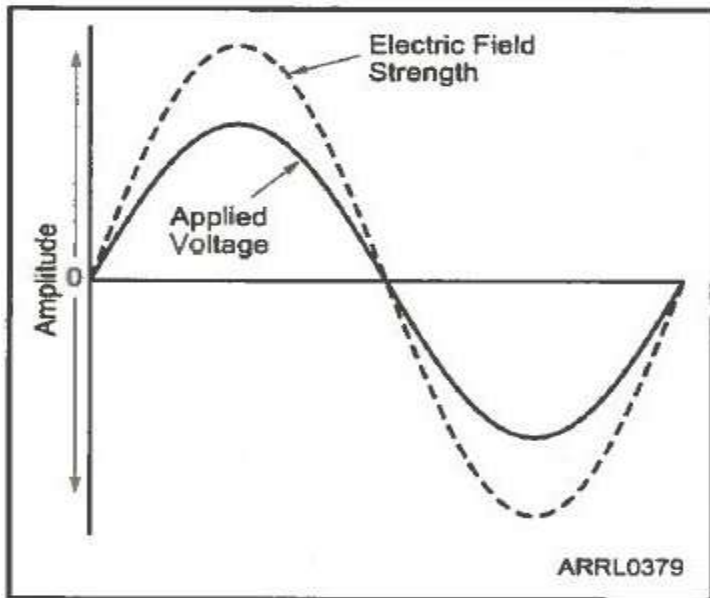- Max current at 0 volts
- 0 current at Maximum volts
- Current leads voltage (ICE)




Voltage/Current Relationship in Inductors

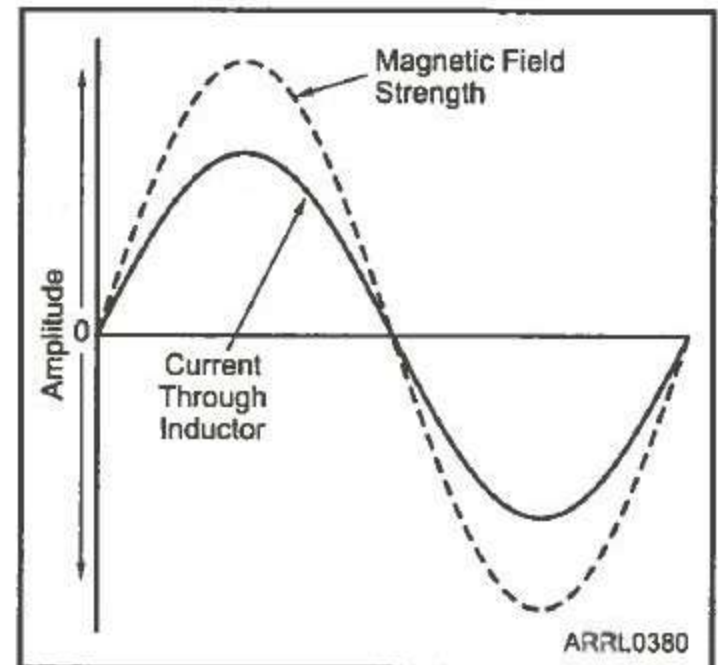- Inductors **resist** changes in current
 - Physical example, flywheel
- Relationship between AC voltage and current (in an inductor) complements that in a capacitor
 - Stored Magnetic (field) energy is in phase with current



Back EMF (induced voltage) in Inductors

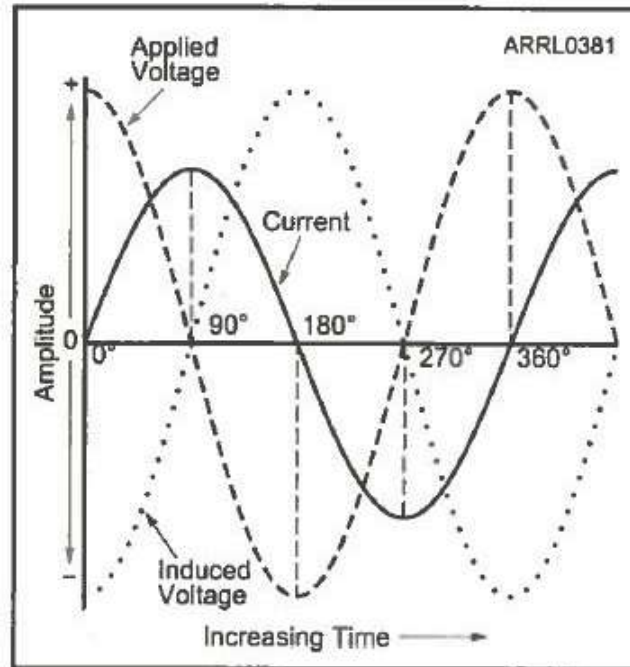
- is greatest when the magnetic field is changing the fastest
- is generated with a polarity that opposes the change in current



AC Voltage/Current phase relationship in Inductors

ELI - current LAGS voltage (V_L)

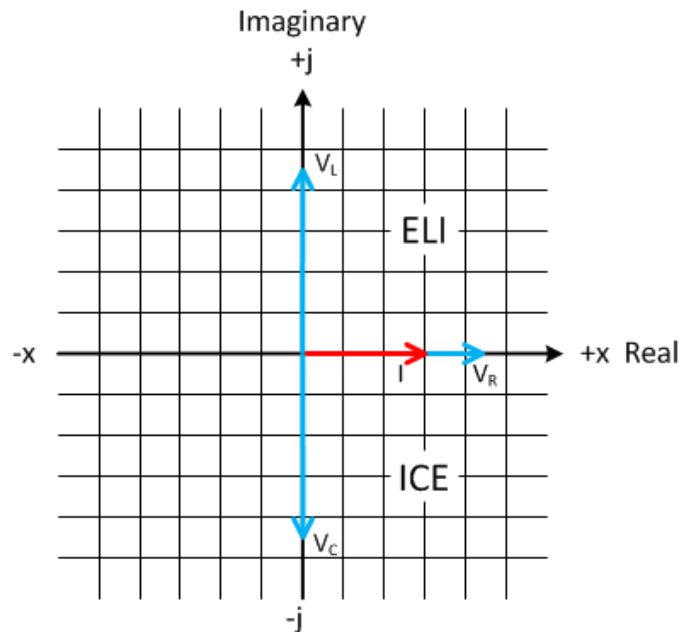- voltage(V_L) **LEADS** current
- (current is reference) phase angle is $+90^\circ$



Resistance versus Reactance

- Resistance is the opposition to the passage of (DC or AC) current (ohm Ω)
- Reactance is the opposition to the AC current flow through an inductor or capacitance
 - Inductive reactance
 - Capacitive reactance

Inductive Reactance

- Increases with increasing frequency

- $X_L = 2\pi f L$

where

X_L = reactance in ohms

f = frequency in hertz

L = inductance in henries

Capacitive Reactance

- Increases with decreasing frequency

- $X_C = 1/2\pi f C$

where

X_C = reactance in ohms


f = frequency in hertz

C = capacitance in farads

Complex Impedance


- Impedance (Z) is composed of two components, resistance and reactance
- Reactance can be either inductive or capacitive
- Resistance and Reactance may be connected either in series or parallel

Series Circuit

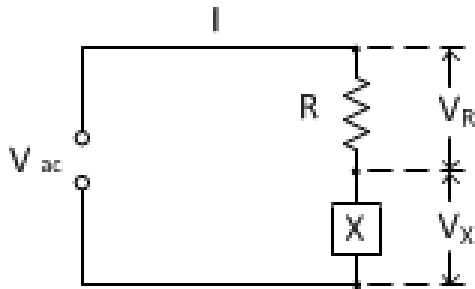

- Current (I) is the same through both elements (R & X)
 - $I = I_R = I_X$
- Voltages (across the elements) are different (V_R & V_X)
 - $V_{ac} = V_R + V_X$

Parallel Circuit

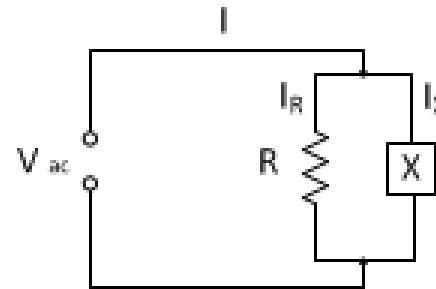

- Voltage (V_{ac}) is the same across both elements (R & X)
 - $V_{ac} = V_R = V_X$
- Currents (through each element) are different (I_R & I_X)
 - $I = I_R + I_X$

Complex Impedance


The phase relationship between the current (I) and voltage (for the whole circuit, V_{ac}) can be between 0° and $\pm 90^\circ$

- The phase angle depends on the relative amounts of resistance and reactance
- The sign of the angle depends on the type of the reactive element
 - Inductive reactance produces a positive angle
 - Capacitive reactance produces a negative angle

Reduce multiple elements to one equivalent element

- Multiple resistors to one resistor
- Multiple reactive elements (capacitors / inductors) to one reactive element
 - Capacitors (-90°) and inductors ($+90^\circ$) have opposite phase angles
 - Combining capacitors and inductors will result in a smaller TOTAL reactance (adding the negative and positive angles will cancel each other)
 - If the capacitors and inductors have EQUIVALENT reactive values, they will cancel each other (angle= 0° thus $X=0$), resulting in only a resistive element (R)


Calculate Impedance

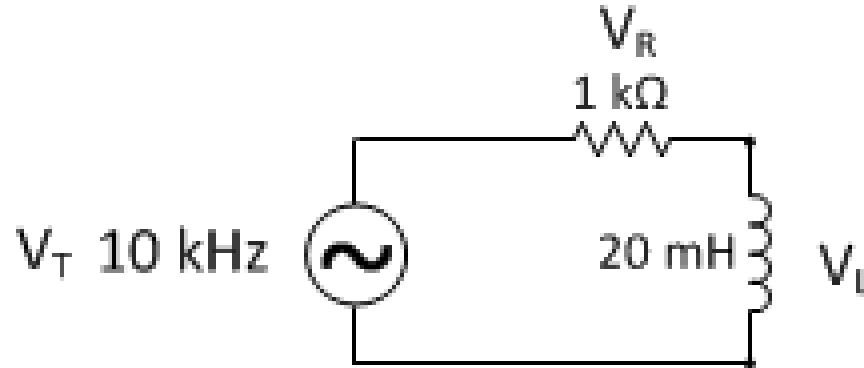

Calculate Reactance of 20 mH inductor at 10 kHz


- $X_L = 2\pi f L$
- $X_L = 2 \times 3.14 \times (10 \times 10^3) \times (20 \times 10^{-3})$
- $X_L = 1256\Omega$

Calculate Impedance

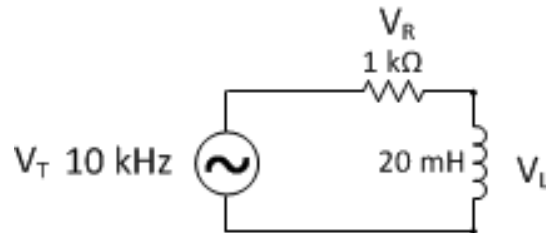


Since we aren't given a V_T , we assume $I=1$

- $V_R = 1000\text{v}$ (voltage in phase with current)
- $V_L = 1256\text{v}$ (voltage leads current by 90° , "ELI")
- $V_T = \sqrt{1000^2 + 1256^2} = 1605$
- $\theta = \tan^{-1}\left(\frac{\text{opp}}{\text{adj}}\right) = \tan^{-1}\left(\frac{1256}{1000}\right) = 51.5^\circ$
- $V_T = 1605 \angle 51.5^\circ$
- $Z = \frac{V_T}{I} = \frac{1605 \angle 51.5^\circ}{1 \angle 0^\circ} = 1605 \angle 51.5^\circ \Omega$

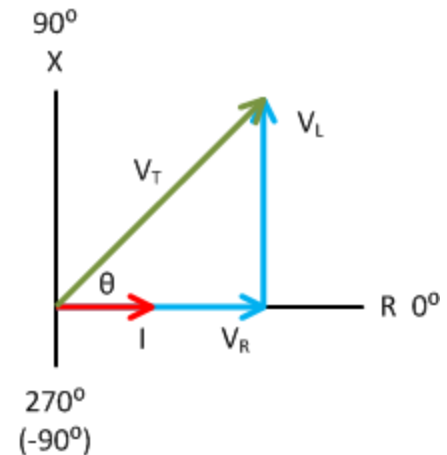


Calculate Impedance

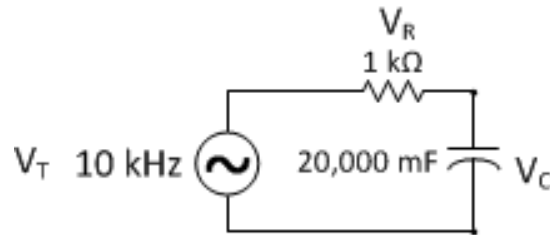

What if we would have had a 20,000 mF capacitor?

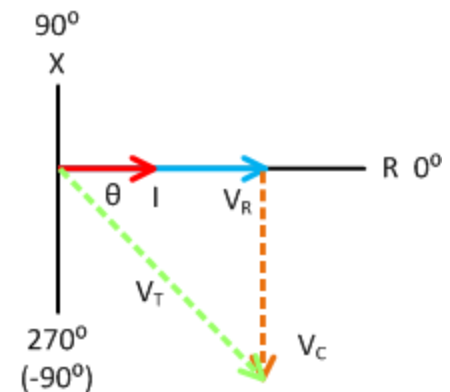- $X_C = 1/(2\pi f C)$
- $X_C = 1/[2 \times 3.14 \times (10 \times 10^3) \times (20,000 \times 10^{-6})]$
- $X_C = 1/1256\Omega = 1256\angle -90^\circ$
- voltage lags current by 90°
- OR current leads voltage by 90° , “ICE”
- $Z = 1605\angle -51.5^\circ \Omega$



Calculating Impedances and Phase Angles - BASIC Rules

- Impedances in series add together
- Admittance is the reciprocal of impedance

$$Y = \frac{1}{Z}$$

- Admittances in parallel add together
- Inductive and capacitive reactance in series cancel
- $\frac{1}{j} = -j$

Refresher

- Conductivity (G) is the reciprocal of Resistance (R)

$$G = \frac{1}{R} \text{ units of siemens (S)}$$

- Susceptance (B) is the reciprocal of Reactance (Y)


$$B = \frac{1}{Y} \text{ units of siemens (S)}$$

- Taking the reciprocal of an angle, changes its sign

$$37^\circ = \frac{1}{-37^\circ} \quad \text{and} \quad -73^\circ = \frac{1}{73^\circ}$$

Refresher (cont)

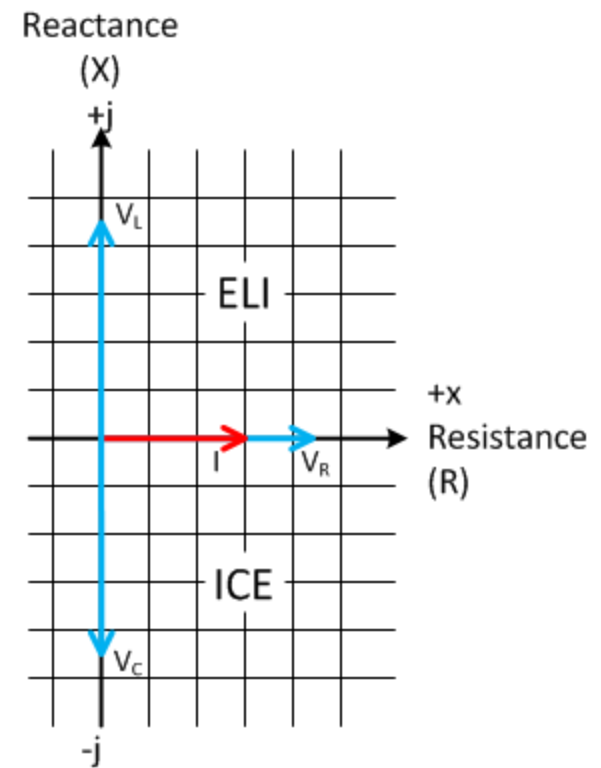
- Voltage determines the reference for phase angle
 - Current is the reference
 - If voltage LEADS current (ELI) -> Positive phase angle
 - If voltage LAGS current (ICE) -> Negative phase angle
 - Voltage LAGS current = current leads voltage



Reactive Power and Power Factor

- Power = Voltage x Current (DC circuit)
- Reactive Power = Voltage_{RMS} x Current_{RMS}
 - AC circuit, when voltage & current are in phase
- Apparent Power
 - Does not take into consideration phase angle
 - Expressed in units of volt-amperes (VA)
 - AKA reactive, nonproductive or wattless power (VAR)

Power Factor

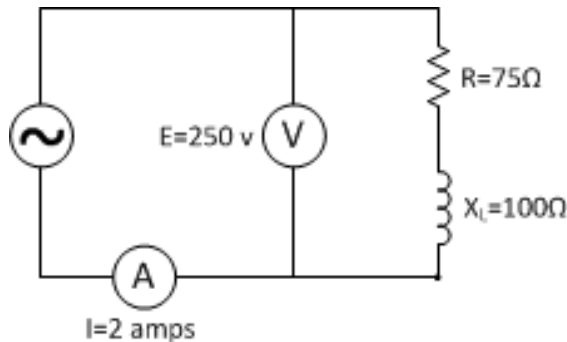

$$PF = \frac{P_{REAL}}{P_{APPARENT}}$$

- Apparent power = 250 V x 2 A = 500 VA
- Real power = $I^2 R = (2 \text{ A})^2 \times 75 \Omega = 300 \text{ W}$
- $PF = \frac{Real}{Apparent} = \frac{300 \text{ W}}{500 \text{ VA}} = 0.6$
- Power Factor is calculated using phase angle (θ) between the current and voltage [PF= Cos (θ)]
 - PF = 1 when $\theta = 0^\circ$ (all apparent power is real power)
 - PF = 0 when $\theta = 90^\circ$ (all apparent power is reactive power)

Resonant Circuits

- Circuits with different inductive and capacitive reactances


- Series – different voltages
- Parallel – different currents

- Circuit is said to be resonant when $X_L = X_C$

- Series – V_C will cancel V_L , leaving only V_R
- Parallel – I_C will cancel I_L , leaving only I_R

- Calculation of Resonant frequency

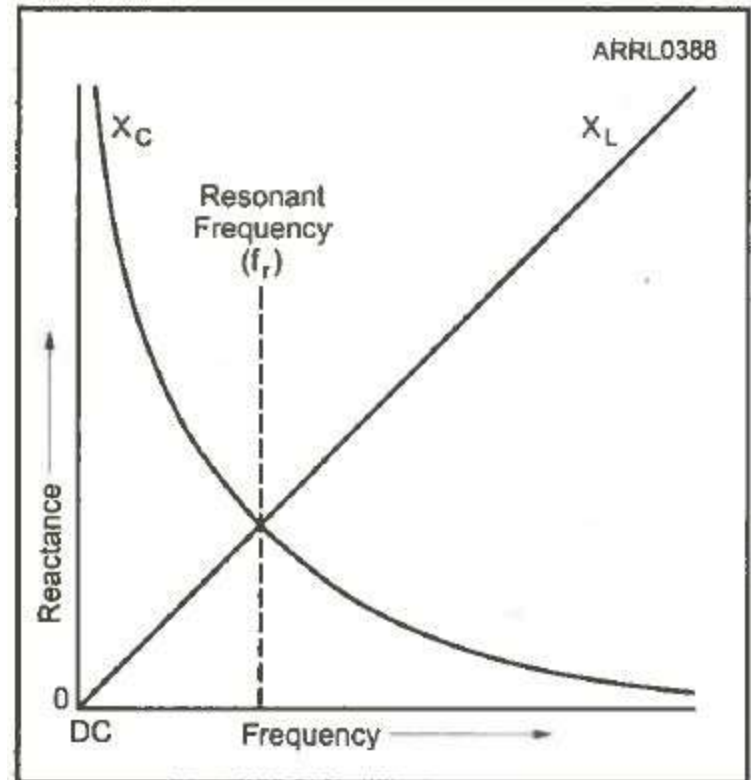
- $X_L = X_C$
- $2\pi f L = 1/2\pi f C$
- Resonant frequency (f_r) = $\frac{1}{2\pi \sqrt{LC}}$



Impedance of Resonant Series Circuits

Series Circuits

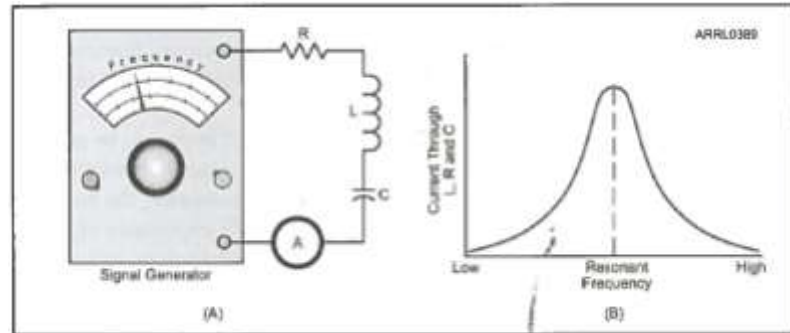- Same current
- V_L is 180° out of phase with V_C




- At resonant
 - $V_L = V_C$
 - Equal amounts of energy are stored in each component
 - The energy being supplied will cause voltages across the inductor and capacitor to build to multiple times the source voltage
 - X_L cancels X_C , resulting in maximum current
 - Voltage and current are in phase

Impedance of Resonant Parallel Circuits

Parallel Circuits

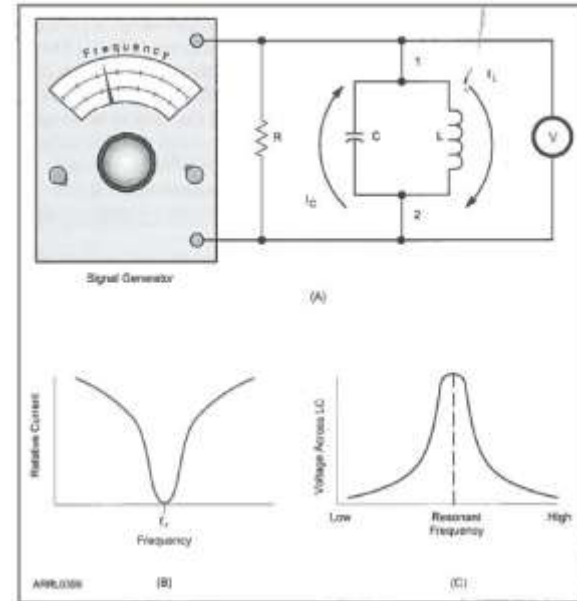- Same voltage
- I_C is 180° out of phase with I_L




- At resonant
 - $I_L = I_C$
 - $I = (I_L + I_C) = 0$, so the parallel combination will appear like an open circuit
 - The energy being exchanged between the inductor and capacitor will result in large circulating current
 - Total current from the generator is small
 - Voltage (across the tank) is at maximum
 - Voltage and current are in phase

Q and Bandwidth of Resonant Circuits

- Practical components

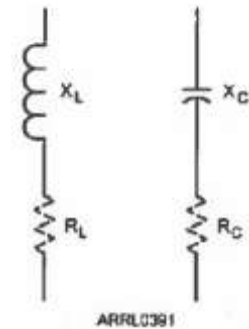- Can be represented as ideal components (inductor or capacitor) in series with a resistor
- That resistance dissipates some of the stored energy




- Quality factor (Q)

- Represents how close to an ideal component is the practical component

- $Q = \frac{X}{R}$

- Ratio of how much energy is stored to how much energy is dissipated

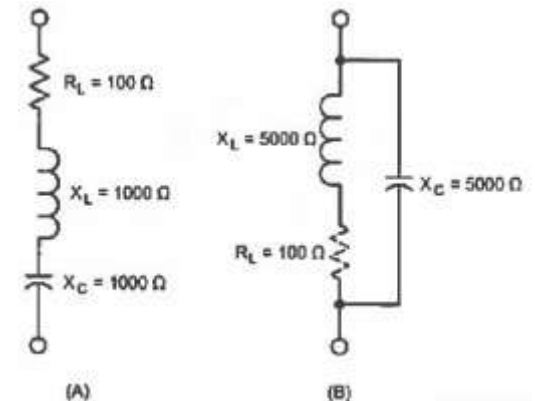- Energy losses of a capacitor is usually much less than that for an inductor




- Thus the Q of the inductor is usually the limiting factor of the Q of a resonant circuit

- The only way to raise the Q of an inductor or capacitor is by using components with less internal resistance

Q and Bandwidth of Resonant Circuits (cont)

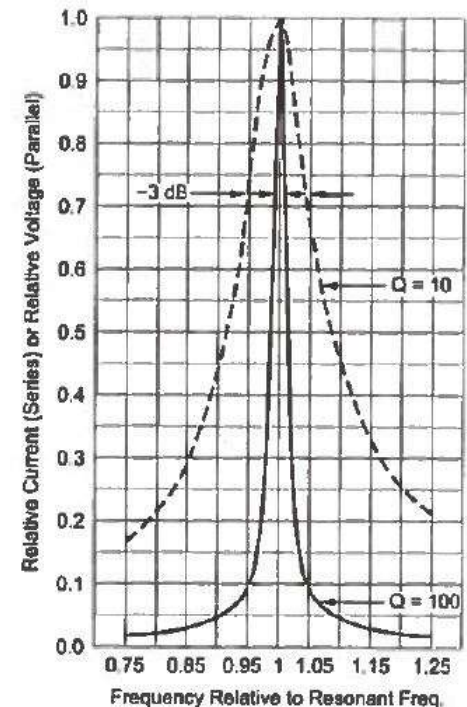- Resonant Circuit Bandwidth
 - Bandwidth of the frequency range where the voltage (or current) is no more than 3 dB (i.e. .707) below the peak
 - Also called the half-power (or -3 dB) bandwidth
 - $\Delta f = \frac{f_r}{Q}$
 - Δf = the half power bandwidth
 - f_r = the resonant frequency of the circuit
 - Q = the circuit Q
 - Higher Q, the narrower the bandwidth (sharper)



Q and Bandwidth of Resonant Circuits (cont)

- Skin Effect and Q
 - As frequency increases
 - more of the current travels closer to the surface of the wire
 - the “effective” resistance of the wire increases
 - HF – outer few thousandths of an inch
 - VHF & UHF – outer few ten-thousandths

Magnetic Cores

- Inductors store magnetic energy, creating reactance
- Wire can be wound around various material
 - Air is relatively inefficient way to store magnetic energy
 - Magnetic material increases the storage of energy (and the inductance)
- Inductance is a function of
 - Number of turns of wire on the core
 - Core materials permeability (air = 1)

Magnetic Cores (cont)

- Select the core material carefully
 - Perform over a desired frequency range
 - Temperature stability
- Core shape
 - Affects magnetic field (shape around the inductor)
 - Magnetic field of one inductor can interact with nearby components (coupling)
 - Toroid cores reduce unwanted coupling by keeping the magnetic field contained in the “donut”

Magnetic Cores (cont)

- Calculating Inductance

- $L = \frac{A_L N^2}{10,000}$

- Or number of turns $N = 100 \sqrt{\frac{L}{A_L}}$

- Each time the wire passes through the core, it counts as a turn

- Ferrite bead

- Small core, slipped over component leads, often used as suppressors for VHF & UHF oscillations

Questions

