

# Four Output Bench Supply

*Every workbench needs a power supply — this one provides four different outputs.*

Larry Cicchinelli, K3PTO



This project is a four output bench power supply. Three outputs (positive voltage) use identical switching regulator circuits that can be set to be any voltage between 3.3 and 20 V. Each output is independent of the others and is capable of up to 1 A. The fourth output is via a negative regulator capable of about 250 mA. The unit I built has two fixed outputs and two variable outputs. You can also make any combination of them variable within the above range.

The only dependence among the outputs is that they are all driven by a single transformer. One of the features of a switching regulator is that you can essentially trade off between voltage and current. The transformer I used is rated at 25 V and 2 A. As such it is good for 50 W. Assuming that the regulator IC being used has an efficiency of 75%, you will have a total of about 37 W available from all power supply outputs. In practical terms this means you can get more current from the outputs than what the transformer is supplying — as long as you stay within the 37 W and the maximum current per regulator.

The regulator I used is the 3.3 V version of the LM2575. If you examine its data sheet you will see that the only difference among the models is the internal voltage divider. This allows you to design a power supply with a higher output voltage by simply inserting a

resistance between the output and the FEEDBACK pin. I selected the 3.3 V version mainly due to its cost relative to the others. With it I can get any voltage from 3.3 V to 20 V from the circuit. You could also use the

“adjustable” version, which will then allow you to select any voltage between 1.23 and 20 V.

The regulator is specified for up to 37 V output. Since I have specified 50 V capacitors, I believe you should be able to get up to about 30 V output. If you want to output a higher voltage than 30 V, I recommend that you use higher voltage capacitors. The transformer I am using is rated at 25 V; however, I have measured the loaded output at closer to 30 V ac, so I could probably get up to 25 V from the regulators. You will also need to use the 200 V range of the digital panel meter (DPM).

There is also a high voltage version of the LM2575 that can provide outputs of up to 57 V. I recommend that you use capacitors rated to at least 100 V if you decide to use that version.

## A Little Theory

Switching regulators come in essentially three varieties: buck, boost and buck-boost.

The regulator in this article is of the buck type — the output voltage is less than the input voltage. The main feature of a switching regulator that differentiates it from a linear regulator is that the switcher oscillates. They generally use a form of pulse width modulation (PWM) in order to regulate the output voltage. The rise and fall times of the oscillator are quite fast and the harmonics can cause interference to communications receivers. This is the reason a spectrum analyzer is one of the pieces of test equipment used to characterize a switching regulator. This is certainly not the case with a linear regulator!

Two of the best tutorials I have found on switching regulators are *Application Note 2031* on the Maxim-IC Web site at [www.maxim-ic.com/appnotes.cfm/an\\_pk/2031](http://www.maxim-ic.com/appnotes.cfm/an_pk/2031) and at [www.national.com/appinfo/power/files/f5.pdf](http://www.national.com/appinfo/power/files/f5.pdf) from National Semiconductor. Rather than try to repeat much of the material in that note, I suggest that you get a copy and read them for yourself.


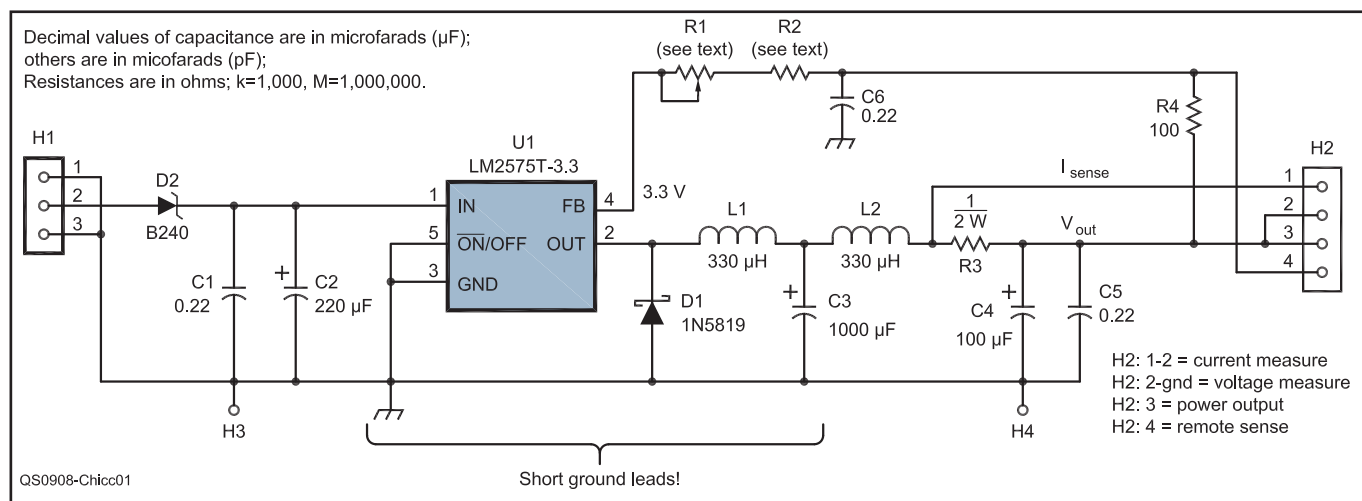


Figure 1 — Schematic diagram of a single positive regulator module.

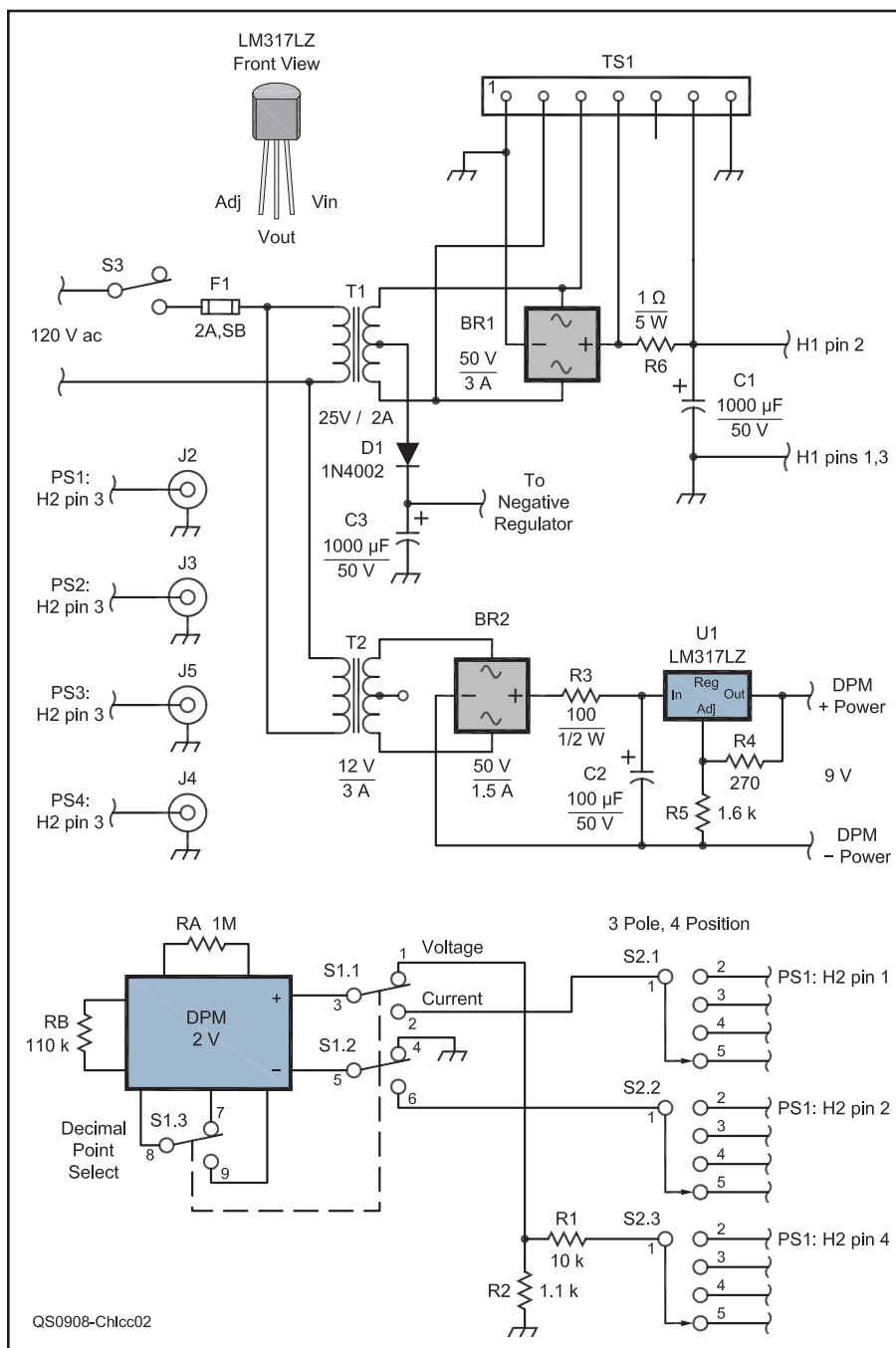

**Figure 2 — Chassis schematic showing the interconnection of the modules as well as control and metering details.**

A switching regulator will have some amount of high frequency noise on its output at the switching frequency, about 52 kHz for the LM2575. In the circuits described here there is a low pass filter on each output that reduces, but does not completely eliminate, this noise. If your requirement is for fixed voltages, you can add a low drop out series regulator (LDO). A good LDO typically requires only about 100 mV between the input and output voltages, so you can design the switcher to be a little higher than the desired voltage and get the benefits of both types of regulators.

### Some Circuit Details

Figure 1 is a schematic of a single positive regulator. There are several variations of the circuit which could be implemented. L2 and C4 are optional. These two components provide a low pass filter that will decrease the high frequency noise that might otherwise appear at the output. The pads for R1 will accommodate a small, multi-turn potentiometer. You can insert one here or you can use the pads to connect a panel mounted potentiometer. If you want a fixed output you can simply short out R1 and use R2 by itself. You can also insert a fixed resistor in the R1 posi-

tion if the calculated value is nonstandard and you want to use two fixed resistors.

The formula for the output voltage (with the 3.3 V version) can be calculated as follows. The current (in mA) through the internal voltage divider is

$$I = 3.3 \text{ V} / 2.7 \text{ k}\Omega = 1.22 \text{ mA}$$

$$R1 + R2 = (V_{OUT} - 3.3) / 1.22 \text{ k}\Omega$$

transposing terms yields:

$$V_{OUT} = [1.22 \times (R1 + R2)] + 3.3$$

Note that if you make  $R1 = R2 = 0$ , the calculation results in an output of 3.3 V. The leakage current of the error amplifier in the regulator is somewhat less than -25 nA, so it can be ignored. Also, since the current for the feedback circuit flows through the current sense resistor, it will be included in the value displayed by the DPM when current is selected.

If you want to have an accurate, fixed output voltage, I recommend selecting a value for R2 that is lower than the calculated value. Then select a potentiometer for R1 that yields a reasonable adjustment range.

If you decide to use the extra LC filter, you will have to install L1 and L2 such that their phasing dots line up with the dot symbols on the circuit board. I found out the hard way that if the dots are at the same end of the board, the output will have an additional low frequency ripple. When I built my board I just happened to have three circuits assembled correctly. The fourth one had a serious low frequency ripple that I could not get rid of. I eventually replaced every component, one at a time, to find the bad one. When I replaced L2 the output was okay. It was then I noticed the phasing dots. I reversed L2 just to see what would happen and the ripple came back. There can be inductive coupling, even though there is a ground plane on both sides of the board under the inductors.

### Remote Sensing

A feature of many power supplies is that of remote sensing. This is used to electronically adjust for the voltage drop in the wires carrying current to the load. I found that, even with relatively short wires, there can be significant voltage drop between the regulator and its load. There is provision for remote sensing in this circuit. If you are not going to use remote sensing then you should insert a jumper in place of R4. R4 (100 Ω) is there for protection just in case the remote sense connection is missing.

To do remote sensing most effectively you will have to implement the circuit somewhat differently than is indicated in the chassis schematic. I used the same point to pick up the output voltage for both the voltage and current measurements (H2-2). This measures the voltage at the output of the regulator board — not at the load. If you want really

accurate readings on the DPM, and have accurate remote sensing, you will have to pick up the voltage measurement from the remote sense input of the board at H2-4 (see Figure 2). This will involve using a three pole, four position rotary switch. This is necessary because you still need to measure the voltage drop across the current sense resistor right at the resistor.

If you do not want to use remote sensing you can simplify the switch wiring to use a two pole switch instead of the three pole listed. In this case you would essentially not use S2.2 and connect S1.2 to the common of S2.3 instead of S2.2.


Strictly speaking even this does not fully implement remote sensing. This circuit does not have a mechanism to adjust for the voltage drop in the ground leg. Most high-end commercial supplies will have both power and ground sense inputs. For this power supply make sure that the ground leads have minimal voltage drop. Measurements inside the chassis have indicated this. I have measured about 100 mV drop at 1 A between the positive output of the regulator board and the chassis connector. There was no measurable voltage drop in the ground circuit. You just have to be sure to use relatively heavy wires for the ground connections.

## Efficiency

Table 1 on the binaries web version shows the efficiency of the positive regulator with various input voltages. Notice that the efficiency is really good at 14 V; however, the circuit is no longer regulating! Optimum efficiency seems to occur at 20 V but there is not a whole lot of variation between 16 and 28 V.

## Rectifier Circuit

Figure 2 shows the connections among the parts of the system — regulator boards, DPM and rectifier circuit. The components

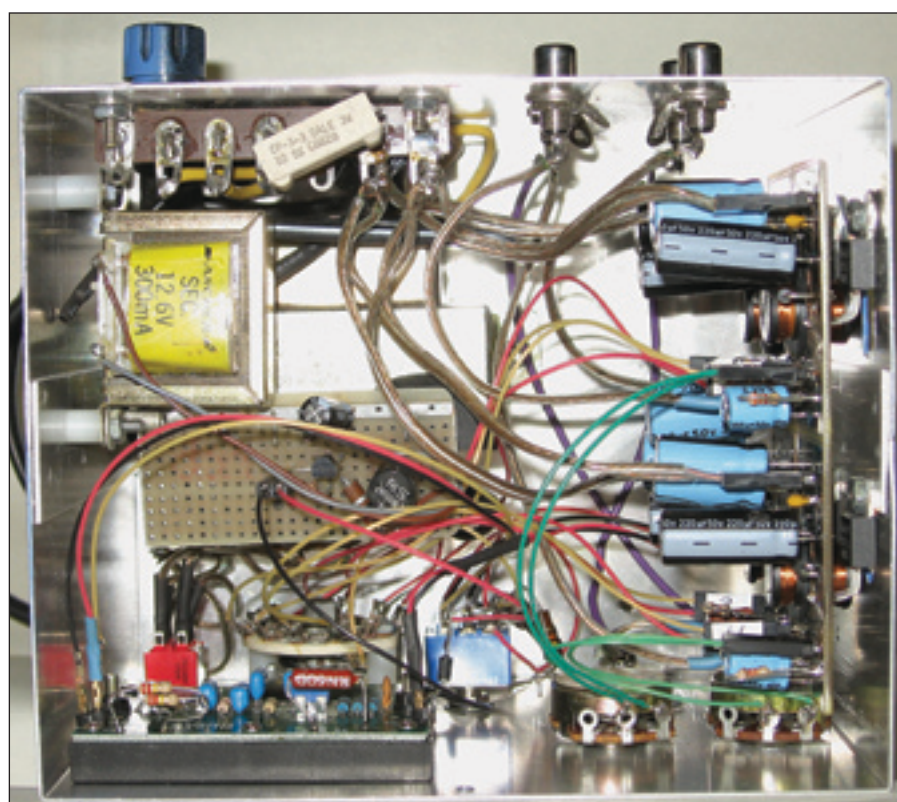


**Figure 3 — Underchassis view of the completed power supply. The components used for the main rectifier circuit are mounted on a terminal strip shown at the top left.**

used for the main rectifier circuit are mounted on a terminal strip (Mouser 158-1008). You can see the terminal strip and R6 at the top left of Figure 3. You can hardly see it, but C1 is mounted underneath the terminal strip. The leads of the bridge rectifier are soldered into the holes that are used to rivet the terminals to the Bakelite. One of the four leads, the negative output, is soldered to a grounded terminal. Since I have had quite a few of these terminal strips for several years I used fine Emory paper to clean their surfaces as well as a small file to clean the holes. This was done

in order to insure good solder connections.

## Negative Regulator

The negative regulator is of the buck-boost configuration. It converts a positive voltage into a negative one (see Figure 4). This design uses many of the same component values as the positive regulators. I was unable to implement the current measuring circuit within a feedback loop. I tried several configurations but each introduced a significant low frequency noise component to the output voltage. There was also some

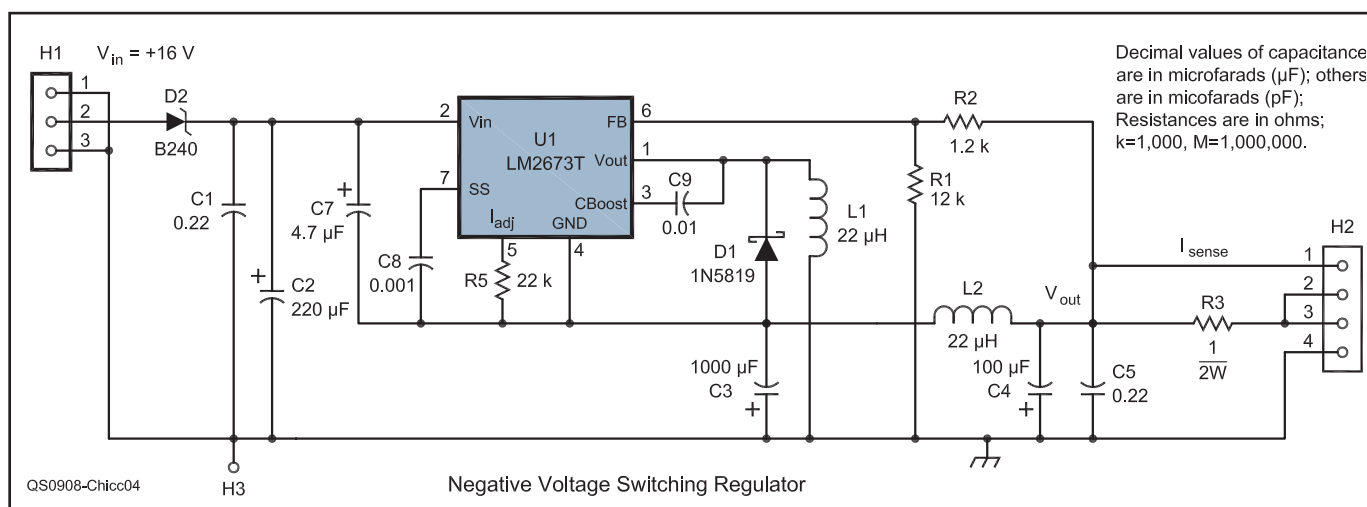

**Figure 4 — Schematic diagram of a single negative regulator module. The complete supply can include up to four modules.**

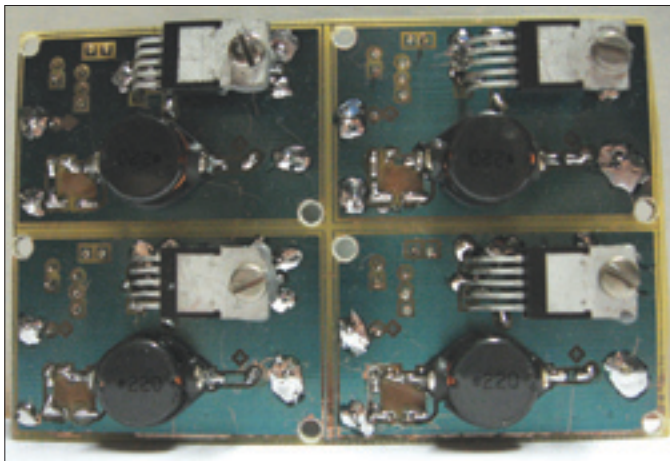


**Table 1**  
**Power Supply Efficiency Using the Positive Regulator with  $R_{LOAD}$  of 50  $\Omega$**

<i>Measured Values</i>			<i>Calculated Values</i>		
Voltage In	Current	Voltage Out	Power In	Power Out	Efficiency (%)
14	0.275	13.7	3.85	3.75	98
16	0.25	12.6	4	3.18	79
18	0.23	12.6	4.14	3.18	77
20	0.2	12.6	4	3.18	79
22	0.19	12.6	4.18	3.18	76
24	0.175	12.6	4.2	3.18	76
26	0.165	12.6	4.29	3.18	74
28	0.155	12.6	4.34	3.18	73

**Table 2**  
**Power Supply Efficiency Using the Negative Regulator with  $R_{LOAD}$  of 50  $\Omega$**

<i>Measured Values</i>			<i>Calculated Values</i>		
Voltage In	Current	Voltage Out	Power In	Power Out	Efficiency (%)
5	1.3	11.1	6.50	2.46	38
7	0.77	12.1	5.39	2.93	54
9	0.48	12.2	4.32	2.98	69
11	0.38	12.2	4.18	2.98	71
13	0.32	12.3	4.16	3.03	73
15	0.27	12.3	4.05	3.03	75
16	0.25	12.3	4.00	3.03	76



**Figure 5 — Back side of the PCB assembly with the ICs folded over and the bolts holding the nuts in place while the epoxy hardens.**

50 kHz noise present on the output, so I implemented an additional low pass filter on the output that reduces it considerably.

The negative regulator uses a different rectifier than the positive regulators. This was necessary because the LM2575 has a maximum input to output voltage specification of 40 V. Since the output of the main bridge circuit is 30 V and the output of the negative regulator is -12 V, the difference exceeds the specification. Using the center tap of the transformer yields close to +16 V for the negative regulator. The half wave rectifier circuit is not as efficient as a bridge, but it will suffice for bench top analog circuits. The components can be mounted to the unused terminals of the terminal strip used for the main rectifier.

One surprising parameter of this circuit is that the inductor current is quite high. Even with no load, the formula indicates that there

will be about 200 mA flowing through it. With a 100 mA load there will be an increase of about 175 mA. You can find the formula on page 20 of the LM2575 data sheet. These current values may be surprising to you, since the input and output currents are roughly the same with a 16 V input. The cited references show why this happens — the input voltage is applied across the inductor for 50% of the time.

This circuit also has a significant turn-on surge current. I found that the circuit will not turn on if a relatively heavy load is connected and the input voltage is current limited. I discovered this while testing the circuit and it was being driven by one of the positive regulators. There was no problem with it being driven from the rectifier circuit.

Table 2 is a chart showing the efficiency of the negative regulator with various input voltages. As you can easily see, the efficiency

is much better with an input voltage of at least 9 V.

## The Digital Panel Meter

Another feature of the unit is the digital panel meter (DPM). It can be switched to measure the output voltage (H2 pin 1 to ground) as well as the current drawn (voltage between H2 pins 1 and 2) for each of the positive supplies. Figure 2 shows the circuit I implemented. A three pole, four position rotary switch selects which power supply is being monitored and a three pole, double throw toggle switch selects between voltage and current measurements.

The DPM is a 2000 count unit with a basic range of 200 mV. It does not have a 2 V range. I inserted my own resistors on the DPM board for RA (1 M $\Omega$ ) and RB (111 k $\Omega$ ). In order to get a 10:1 voltage ratio the resistor ratio needs to be 9:1. If you have to do this for your DPM, you will want to insure that you maintain the accuracy of the meter. I strongly suggest that you maintain at least a 1 M $\Omega$  input resistance so that it does not affect the external voltage divider used for measuring the voltage. I used the calibration potentiometer on the DPM for the final accuracy adjustment. I borrowed a four digit DVM of known accuracy to insure good calibration.

It may be hard to get two resistors with exactly a 9:1 ratio from your “junk box.” On the DPM I used two 220 k $\Omega$  resistors in parallel to get the required 111 k $\Omega$  resistance. By measuring several 220 k $\Omega$  resistors I was able to find a combination that was quite close to 111 k $\Omega$ . For the voltage measuring divider you can do the same thing using a 10 k $\Omega$  input resistor and then a 1 k $\Omega$  and 110  $\Omega$  in series for the “low” side of the divider. The parts list specifies 1% resistors, in case you don’t want to combine resistors as I did.

In order to measure the voltage drop across the 1  $\Omega$  current sense resistors, the DPM needs either an isolated power supply or some more circuitry (which could require another power supply anyway). For this system I selected the isolated power supply implementation. I used a series regulator because they are somewhat easier to implement and because the DPM has a very low current requirement. Rather than build another printed circuit board I decided to mount all the components, except the transformer, on a breadboard.

The DPM also has a set of jumpers that allow selection of the decimal point location. As can be seen on Figure 2, I use one pole of the toggle switch to select those inputs.

## Some Construction Hints

On the DPM and the regulator boards, I used pin headers for all of the connections that come off the boards. (see the parts list