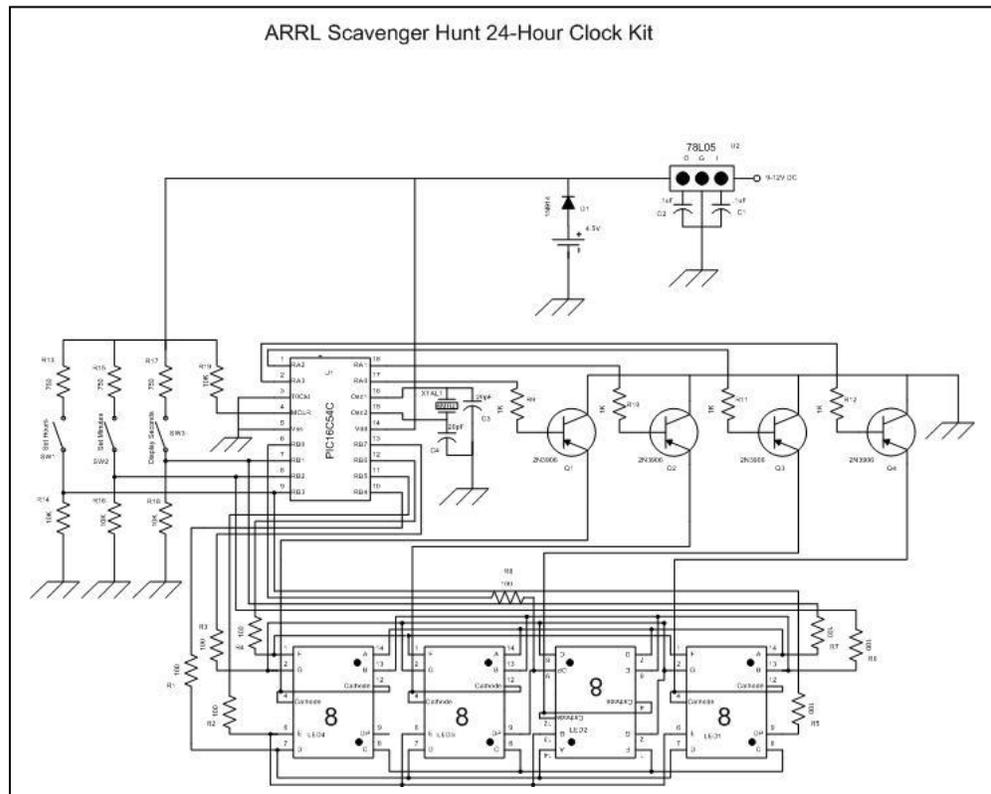




How the ARRL ETP Solder 101 24-Hour Clock Kit Works

This is the circuit diagram of the clock. We will break this circuit down into sections and discuss the operation of each section.




© Copyright 2010-2013 American Radio Relay League, Inc. all rights reserved. This content is intended for educational purposes. When used for this purpose, please acknowledge ARRL as the source. Additional permission is required to use this material in any training or product that will be redistributed or used for re-sale.




How the ARRL ETP Solder 101 24-Hour Clock Kit Works

Power Supply

There are two sources of power for the clock, the 9 to 12 volt DC “wal-wart” (primary) and 3-AA Battery cells (backup). The clock draws approximately 20mA of current at 5 volts. The power supply circuit consists of the voltage regulator, U2, that steps down the 9 to 12 volts DC from the “wal-wart” to the 5 volts required for the circuit. The capacitors C1 and C2 are filter capacitors to help mitigate any

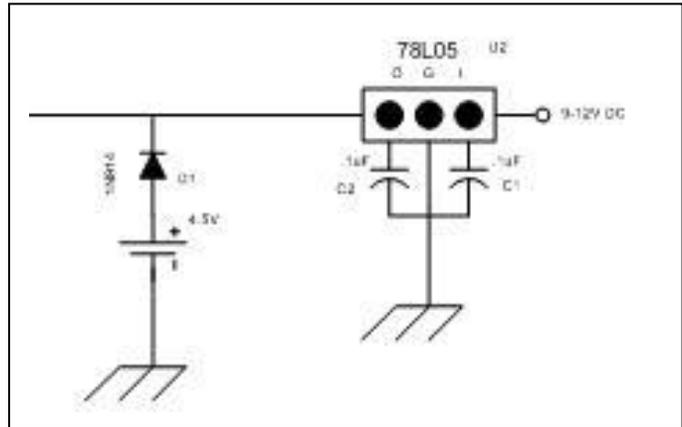

“noise” generated by the regulator as it responds to current demand transients. The backup battery pack (which is 3-AA cells in series and supplies a voltage of 4.5 volts with fresh batteries) is isolated from the output of the voltage regulator by the diode D1. During normal operation, the cathode side of D1 has 5 volts and the anode side has 4.5 volts, this is a reversed biased condition and the diode is in a non-conductive state. In other words, the current from the regulator powers the circuit. When there is a power failure and the “wal-wart” shuts down, the voltage from the regulator on the cathode side of D1 is zero volts and the anode side has the 4.5 volts from the battery. In this case D1 is forward biased, and the diode conducts and connects the batteries to the circuit to keep the clock operating.

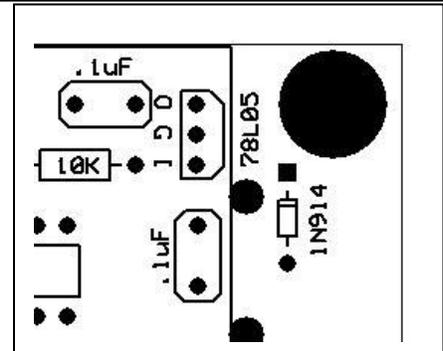




How the ARRL ETP Solder 101 24-Hour Clock Kit Works

The LED displays are made up of 7 LED segments that are turned on as needed for form the digits of time. To display the 4 digits of a 24-hour time would require 28 LED segments (4×7), this number far exceeds the 12 IO lines available on the PIC. To deal with this limitation, the 7 associated LED segments on each digit are connected together and the common cathode of each LED digit are connected to switching transistors thus requiring 11-IO pins. There is also a decimal point on the LED display that is used to make a colon between the hours and minutes of the time display and these decimal points are connected together and use the final IO resource pin. Once the time is computed by the PIC software, the individual digits of the time are converted into a lighting sequence for the individual LED segments that will make up the number. The IO lines are put in a high state (5-volts) and the digit is turned on with the digit control IO pin connected to the common cathode for approximately 4 mSec. The digit is then turned off, the next digit LED segments IO lines are set to high, and the digit is turned on for 4 mSec. The digits are tuned on from right to left (single minute to tens of hour digits) and the process repeated so fast that you will not be able to detect any flicker (but you can see the switching on an oscilloscope display). This process is call multiplexing and the IO pins connected to the bank of 7-segement LEDs is called a data buss.

There is a time interval between when the time digits are turned on of approximately 37uSec. The PIC uses this time to look at 3 IO pins that are connected to switches that allow you to display seconds, and to set the hours and minutes. If a switch is detected being pressed during the 37uSec interval, the program in the PIC jumps to a subprogram to accomplish the desired action (change time or display seconds). When the switch is released, the PIC program resumes the computation and display of time.


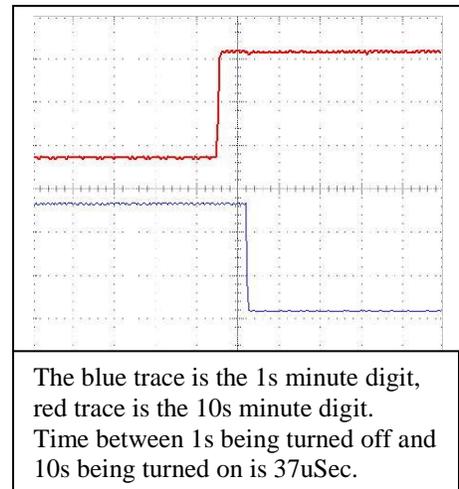




How the ARRL ETP Solder 101 24-Hour Clock Kit Works

Time Setting Switches

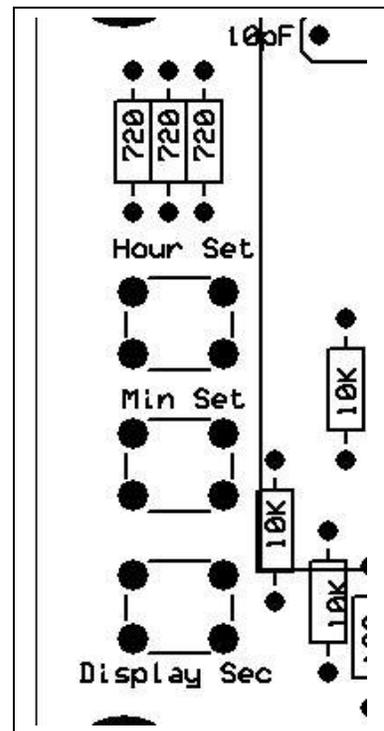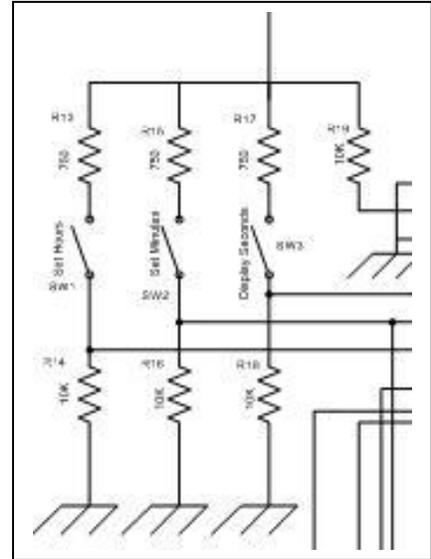The time setting switches, SW1-3, are SPST momentary switches that connect 5 volts to the associated IO pin when the switch is pressed. The resistors in series with each switch are current limiting and voltage dividing resistors so that the appropriate voltage and current level is applied to the IO pin while not drawing excessive current away from the LED segment that shares the IO pin.







How the ARRL ETP Solder 101 24-Hour Clock Kit Works

LED Digits

The 100 ohm resistors are connected to the individual LEDs within the 7-segment display to provide current limiting. The associated segment in each digit is connected together. Notice that the 10s digit of the minute display is installed upside down. This is a neat way of using the decimal points of the 10s digit of the minute display and the 1s digit of the hour display to form a colon to separate the hours numbers from the minutes numbers. The decimal points are programmed to flash at 1 second intervals.

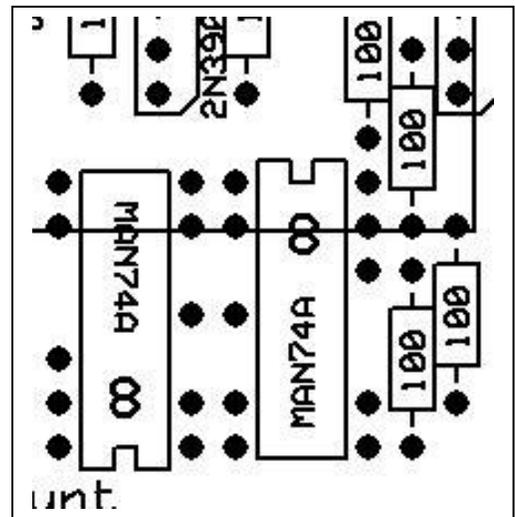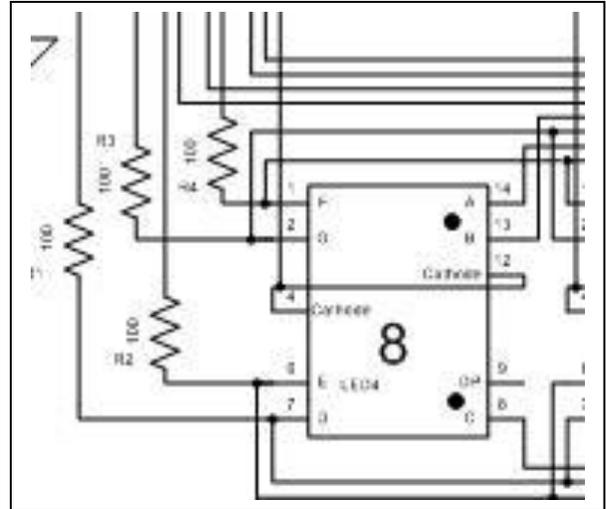



How the ARRL ETP Solder 101 24-Hour Clock Kit Works

LED Digit Turn-on Transistors

The PIC sets up the 7-segment LEDs to display the required number and then the appropriate digit of the display is “flashed” to display the digits from right to left. The current required to illuminate all 7-segments exceeds the current handling capability of a single IO pin. The transistors Q1-4 serve as electronic switches that are turned on and off by the IO pins thereby handling the amount of current.

