

MORSE KEY WIRING DIAGRAM ACTIVITY

Label the parts of the Morse Key and draw the wires that make up the electrical circuit. Use black pencil for black wires and red pencil for red wires. Use arrowheads to show the direction of the flow of electrons through the circuit when active.

